
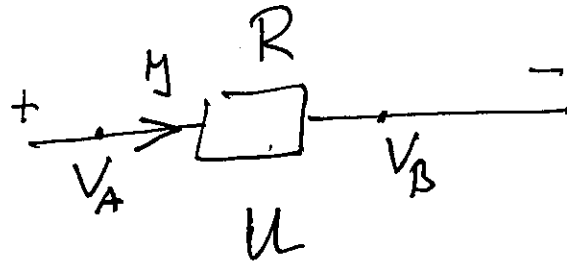


II prova Kirchhoffa.

$$U = IR$$

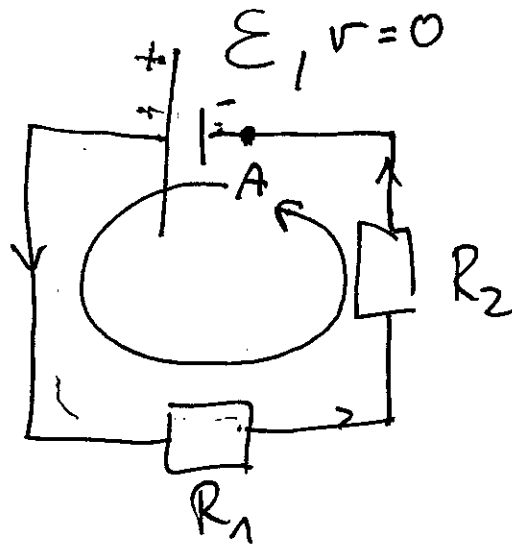


$$V_A > V_B$$




$$\epsilon - IR_1 - IR_2 = 0$$

$$I = \frac{\epsilon}{R_1 + R_2}$$

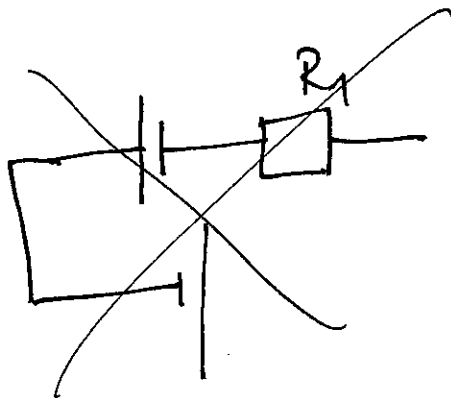

Szukane M_1, M_2, M_3 .

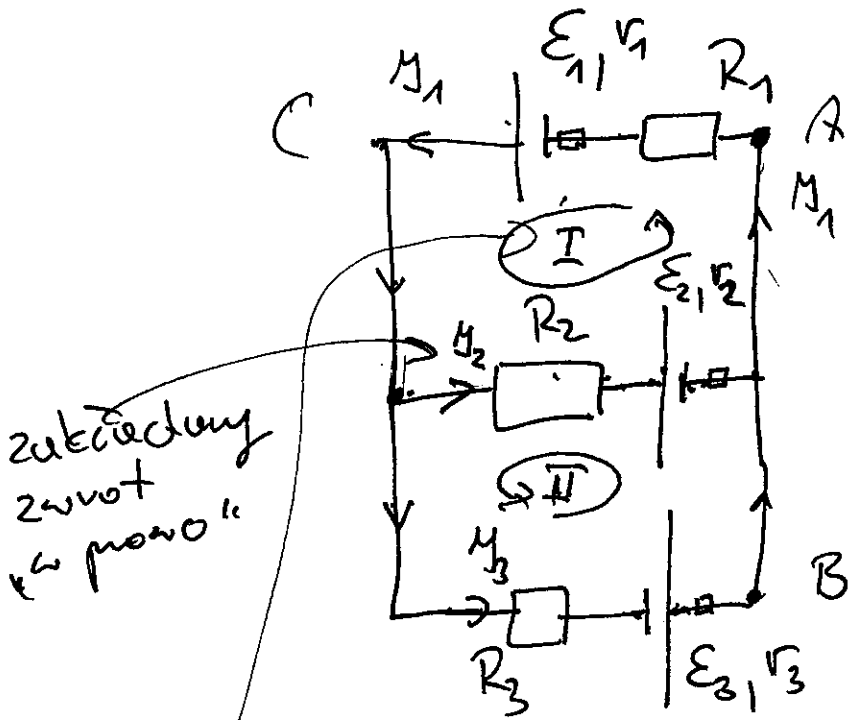

zakładamy
zawrot
prądu

1) $M_1 = M_2 + M_3$ I prąd Kirchhoffa.

dla I.
z A do A

2) $-R_1 M_1 - v_1 M_1 + E_1 - M_2 R_2 - E_2 - M_2 v_2 = 0$


dla II
z B do B

3) $M_2 v_2 + E_2 + M_2 R_2 - M_3 R_3 + E_3 - M_3 v_3 = 0$

"+" bo idziemy
pod prąd.

$U_{AC} = -M_1 R_1 - M_1 v_1 + E_1$ gdy $U_{AC} < 0$ to
 $V_C < V_A$
 i odwrócić.

9.12.

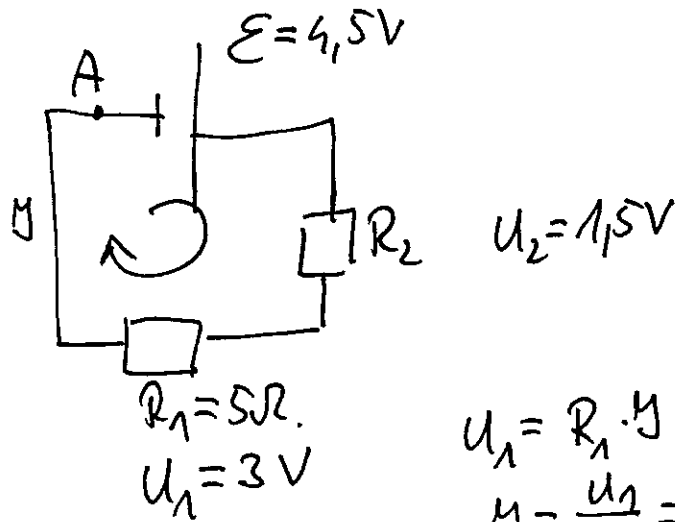

$$U_1 = R_1 \cdot I \Rightarrow \cancel{I = 537 \text{ A}}$$


$$I = \frac{U_1}{R_1} = \frac{3}{5} = 0.6 \text{ A} = I_1 = I_2$$

$$U_2 = R_2 \cdot I \Rightarrow R_2 = \frac{U_2}{I} = \frac{1.5}{0.6} = \underline{\underline{2.5 \Omega}}$$

$$P_1 = U_1 \cdot I_1 = 3 \cdot 0.6 = 1.8 \text{ W}$$

$$P_2 = U_2 \cdot I_2 = 1.5 \cdot 0.6 = 0.9 \text{ W}$$

9.12.

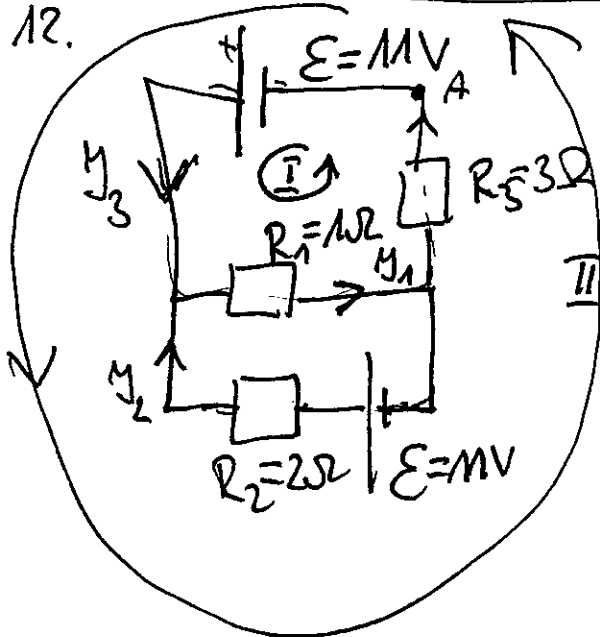

1) $I_3 + I_2 = I_1$ \bar{I} per Kirchhoff

2) 2 A do A per \bar{I}

$$E - I_1 R_1 - I_3 R_3 = 0$$

3) 2 A do A per \bar{II}

$$E + I_2 R_2 - E - I_3 R_3 = 0$$

1) $I_2 + I_3 = I_1$

2) $1 - I_1 - 3I_3 = 0 \Rightarrow I_3 = \frac{1}{3} - \frac{1}{3}I_1$

3) $1 + 2I_2 - 3I_3 = 0$

$$1') \quad \frac{11}{3} - \frac{1}{3} I_1 + I_2 = I_1 \Rightarrow I_2 = \frac{4}{3} I_1 - \frac{11}{3}$$

$$3') \quad 11 + 2I_2 - 3\left(\frac{11}{3} - \frac{1}{3} I_1\right) = 0$$


$$2\left(\frac{4}{3} I_1 - \frac{11}{3}\right) - 11 + I_1 = 0$$

$$\frac{8}{3} I_1 - \frac{22}{3} - 11 + I_1 = 0$$

$$\frac{11}{3} I_1 - \frac{55}{3} = 0$$

$$I_1 = \frac{55}{3} \cdot \frac{3}{11} = \underline{5A}$$

9.18.

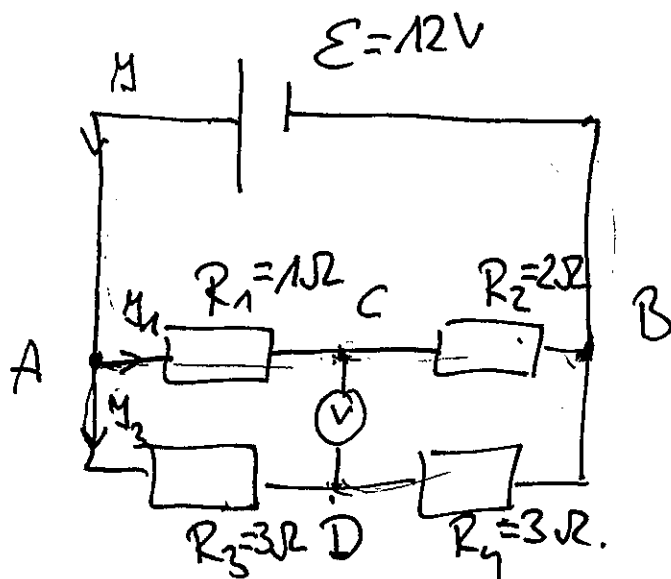

$$-I_1 R_1 - I_1 R_2 + E = 0 \Rightarrow -1 \cdot I_1 - 2I_1 + 12 = 0$$

$$I_1 = \frac{12}{3} = \underline{4A}$$

$$-I_3 R_3 - I_3 R_4 + E = 0 \Rightarrow -3I_3 - 3I_3 + 12 = 0$$

$$I_3 = \underline{2A}$$

$U_{CD} = 2V$ ←

$U_{AC} = -I_1 R_1 = -1 \cdot 4 = -4V$ - ułki w C potencjał jest niższy o 4V od A.

$U_{AD} = -I_3 R_3 = -2 \cdot 3 = -6V$ - w D potencjał jest niższy o 6V od A.

CD. 9.18.

$$U_{CD} = 0 \quad \text{gdy.}$$

$$U_1 = M_1 R_1 = U_3 = M_3 R_3 \Rightarrow M_1 R_1 = M_3 R_3$$

i) jednoczasnie.


$$U_2 = U_4 \Rightarrow$$

$$M_1 R_2 = M_3 R_4$$

dwie strony

$$\frac{M_1 R_1}{M_1 R_2} = \frac{M_3 R_3}{M_3 R_4} \Rightarrow R_4 = \frac{R_3 \cdot R_2}{R_1}$$

9.6.

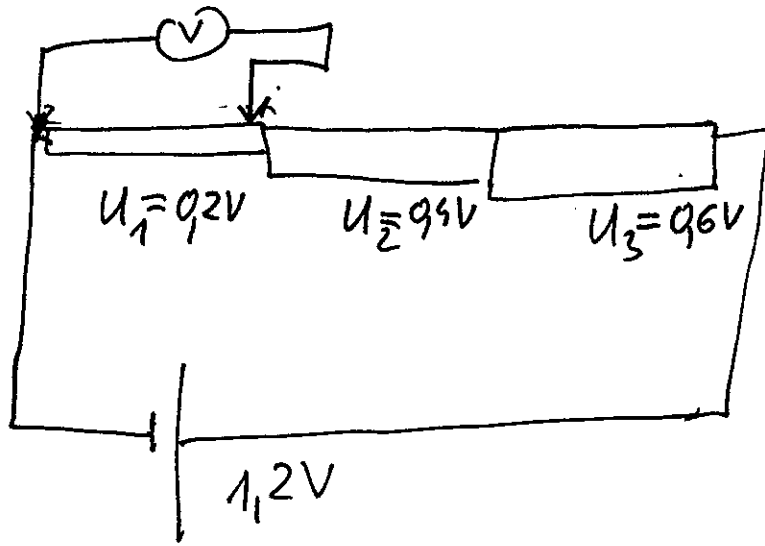

$$I = \frac{U_1}{R_1} = \frac{U_2}{R_2} = \frac{U_3}{R_3} \Rightarrow R_1 = \frac{U_1}{I} \quad R_2 = \frac{U_2}{I} \quad R_3 = \frac{U_3}{I}$$

$$\boxed{R_1 : R_2 : R_3 = U_1 : U_2 : U_3}$$

$$R = \rho \frac{L}{S} \Rightarrow S = \frac{\rho L}{R}$$

$$S_1 = \frac{\rho L}{R_1}$$

$$S_2 = \frac{\rho L}{R_2}$$

$$S_3 = \frac{\rho L}{R_3}$$

$$\frac{S_1}{S_2} = \frac{R_2}{R_1} = \frac{U_2}{U_1}$$

$$\frac{S_2}{S_3} = \frac{R_3}{R_2} = \frac{U_3}{U_2}$$

q.15.

$$Q = m \cdot c \cdot \Delta T$$

$$P \cdot t$$

$$P = \frac{m c \Delta T}{t} = \frac{1 \text{ kg} \cdot 70 \cdot 90}{10 \cdot 80} = 630 \text{ W}$$

$$P = U \cdot I \quad \left\{ I = \frac{U}{R} \right\} \quad P = \frac{U^2}{R}$$

$$Q = P \cdot t \Rightarrow t = \frac{Q}{P} = \frac{Q}{\frac{U^2}{R}} = \frac{Q \cdot R}{U^2}$$

USA $U = 110 \text{ V}$ ayli $\frac{230}{110}$ voy munajsaq.
 ayta cros kedue $\left(\frac{23}{11}\right)^2$ voy oluisuy.


$$t_{USA} = 10 \text{ mi} \cdot \left(\frac{23}{11}\right)^2 = \dots$$

q.16.

$$t = \frac{Q}{P} \Rightarrow \boxed{P_5 = 2 \cdot P_{10}}$$

$$\frac{Q}{P_5} = t_5$$


$$\frac{Q}{P_{10}} = t_{10}$$

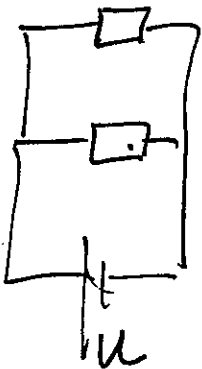

$$P_{\text{vondoytgo}} = P_5 + P_{10}$$

$$t_{\text{vondoytgo}} = \frac{Q}{P_5 + P_{10}} = \frac{1}{\frac{P_5}{Q} + \frac{P_{10}}{Q}} = \frac{1}{\frac{1}{t_5} + \frac{1}{t_{10}}} = \frac{t_5 \cdot t_{10}}{t_5 + t_{10}}$$
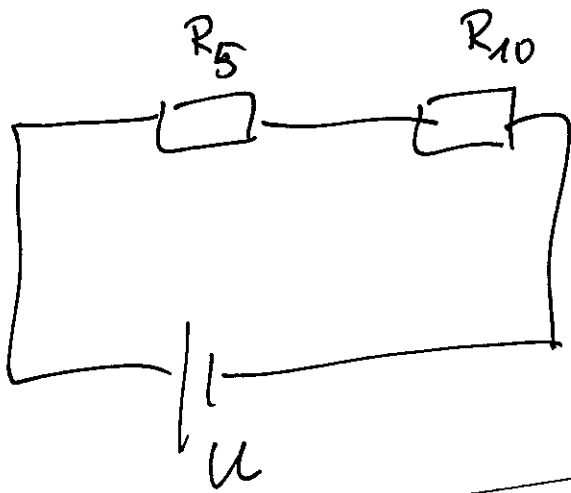
$$\frac{1}{t_{\text{vondoytgo}}} = \frac{1}{t_5} + \frac{1}{t_{10}}$$



$$P_{\text{szeregezo}} = U \cdot I = U \cdot \frac{U}{R_5 + R_{10}}$$

$$P_5 = \frac{U^2}{R_5} \quad P_{10} = \frac{U^2}{R_{10}}$$

$$R_5 = \frac{U^2}{P_5} \quad R_{10} = \frac{U^2}{P_{10}}$$

$$\frac{U^2}{\frac{U^2}{P_5} + \frac{U^2}{P_{10}}} = \frac{U^2}{U^2 \left(\frac{1}{P_5} + \frac{1}{P_{10}} \right)} = \frac{1}{\frac{1}{P_5} + \frac{1}{P_{10}}}$$

$$t_{\text{szeregezo}} = \frac{Q}{\frac{1}{P_5} + \frac{1}{P_{10}}} = Q \cdot \left(\frac{1}{P_5} + \frac{1}{P_{10}} \right) = \frac{Q}{P_5} + \frac{Q}{P_{10}} = t_5 + t_{10} = 1 \text{ Smln.}$$

9.17.

$$P_{\text{mikrofel}} \cdot t_{\text{th}} = Q = m \cdot c \cdot \Delta T$$

$$\Delta T = \frac{P_{\text{mikrofel}} \cdot t_{\text{th}}}{m \cdot c}$$

$$P_{\text{mikrofel}} = U \cdot I_{\text{max vovony}} = U \cdot \frac{Q}{t_{\text{max vovony}}}$$

propennosc

$$Q = I_{\text{max vovony}} \cdot t_{\text{max vovony}}$$

$$P_{\text{mikrofel}} = \frac{3,7 \text{ V} \cdot 720 \text{ mA} \cdot \text{h}}{300 \text{ min} \cdot 5 \text{ h}} = \frac{3,7 \cdot 0,72}{5} = 0,532$$

$$\Delta T = \frac{0,532 \cdot 3600}{1,4 \cdot 4200} = 0,32 \text{ K}$$


3.1. $U = 12V$ $I = 0,12A$

$$R = \frac{U}{I} = \frac{12}{0,12} = 100\Omega$$

$$R = \rho \frac{L}{S} \Rightarrow L = \frac{R \cdot S}{\rho} = \frac{100 \cdot 0,5 \cdot 10^{-6}}{40 \cdot 10^{-6}} = 50 \text{ m}$$

$$S = (0,5 \text{ mm})^2 = 0,5 (10^{-3} \text{ m})^2 = 0,5 \cdot 10^{-6} \text{ m}^2$$

3.2.

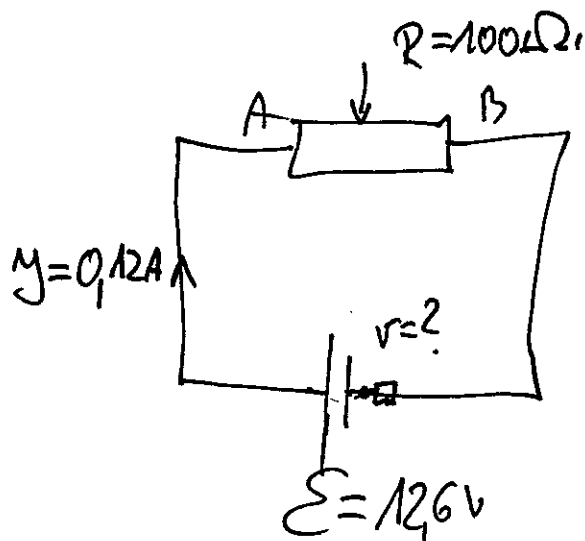

$$E - IR - Ir = 0 \quad \left(I = \frac{E}{R+r} \right)$$


$$\frac{E - IR}{I} = r$$

$$r = \frac{E}{I} - R = \frac{12,6}{0,12} - 100$$

$$r = 105 - 100 = 5\Omega$$

3.3.


$$U_{AB} = 12V$$

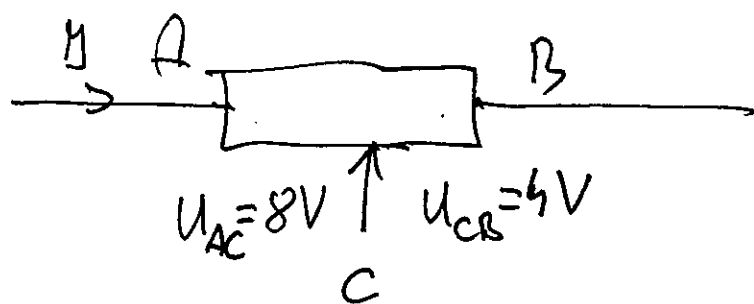

$$I = \frac{U_{AC}}{R_{AC}} = \frac{U_{CB}}{R_{CB}} \Rightarrow \frac{U_{AC}}{\rho \cdot \frac{L_{AC}}{S}} = \frac{U_{CB}}{\rho \cdot \frac{L_{CB}}{S}}$$


$$\frac{L_{AC}}{L_{CB}} = \frac{U_{AC}}{U_{CB}} = \frac{8}{4} = \frac{2}{1}$$

3.4.

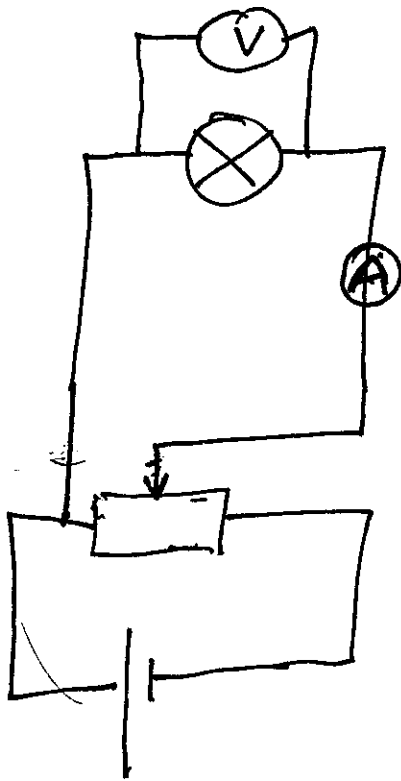

23.1. $P = U \cdot I = U \cdot \frac{U}{R}$

$R = 0,6 \Omega$

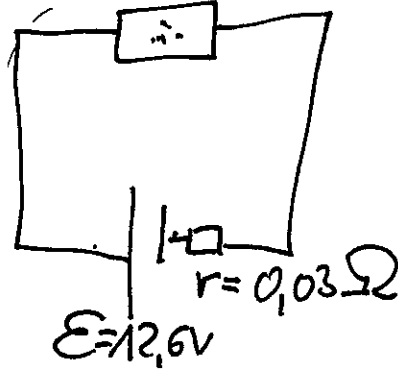


$$I = \frac{\mathcal{E}}{R + r} = \frac{12,6}{0,6 + 0,03} = 20 \text{ A}$$

$$U = I \cdot R = 20 \cdot 0,6 = \underline{12 \text{ V}}$$

$$P = U \cdot I = 20 \cdot 12 = \underline{\underline{240 \text{ W}}}$$

23.2.

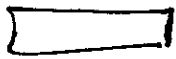

$$R = \rho \frac{L}{S} \Rightarrow \rho = \frac{R S}{L} = \frac{96,4 \cdot 0,1 \cdot 10^{-6}}{0,628} = 3,8 \cdot 10^{-4} \Omega \cdot \text{m}$$

23.3.

$$P = \frac{Q}{t} \Rightarrow t = \frac{Q}{P}$$

$$P = U \cdot I = U \cdot \frac{U}{R} = \frac{U^2}{R}$$

$$t = \frac{Q \cdot R}{U^2}$$

$$t' = \frac{QR}{(0,8 \cdot U)^2} = \frac{QR}{0,64 \cdot U^2} = \frac{1}{0,64} t = 1,56 t$$

Op: t wzrośnie 1,56 razy.
